

Introduction to Verilog design

Lecture 2

ECE 156A

1

Design flow (from the book)


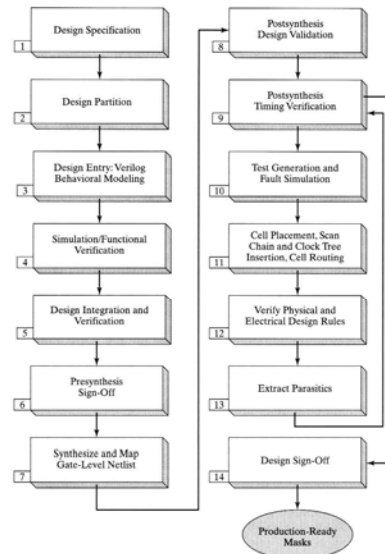


FIGURE 1-1 Design flow for HDL-based ASICs.


2

Hierarchical Design

 

- A chip contain many modules
- A module may contain other modules
 - no recursion
- A module uses predefined cells
- Everything is based on primitives

Hierarchical design flow

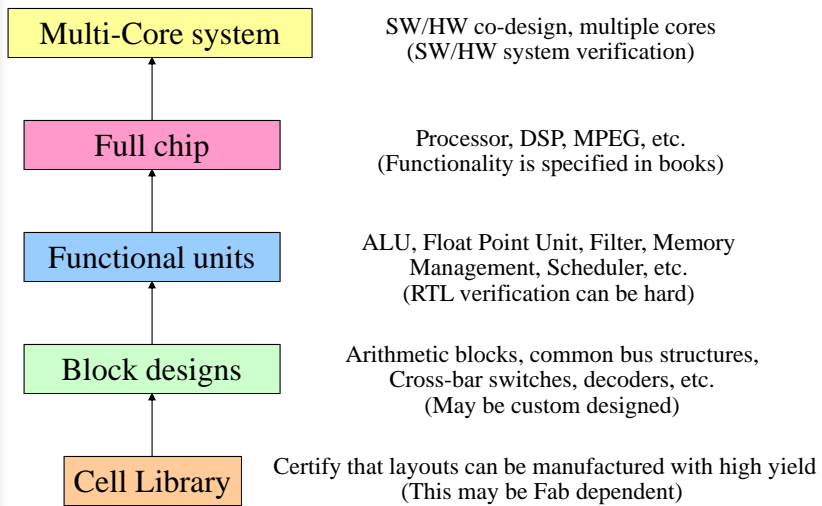

Advantages

- When working at a particular level of design, we don't need to worry about all detail below
 - When putting a system together, you don't need to worry about how a processor is designed
 - Optimization can be done independently at each level
- Since no detail is involved, it is easier to replace the designs with other implementations
 - You can easily change the processor to another implementation without changing the system
 - You can change the technology from 0.45 micron to 0.32 micron without changing the verilog RTL

ECE 156A

5

Primitives and design model

- Verilog includes 26 predefined models of logic gates called primitives
- Primitives are the most basic functional components that can be used to build (*model*) a design
 - Their functions are built into the language by internal truth table
- The output port of a primitive is the first in the list

 


FIGURE 4-1 Schematic and Verilog description of a half adder.

ECE 156A

6

Verilog primitives for combinational logic

n-input	n-output, 3-state
and	buf
nand	not
or	bufif0
nor	bufif1
xor	notif0
xnor	notif1

- n-input: Any number of inputs and 1 output
- n-output: Any number of outputs and 1 input

ECE 156A

7

List of Verilog primitives

- Gates
 - and, nand, or, nor, xor, xnor, buf, not
- Tri-State
 - bufif0, bufif1, notif0, notif1
- MOS
 - nmos, pmos, rnmos, rpmos
- CMOS
 - cmos, rcmos
- Bi-directional
 - tran, tranif0, tranif1, rtran, rtranif0, rtranif1
- Pull
 - pullup, pulldown

ECE 156A

8

Standard cells vs. Primitives

- Verilog primitives are abstract building blocks used to model your design
 - They are not real

- Standard cells are real building blocks used to implement your design
 - Each has a corresponding layout
 - Each has a timing model
 - Cells are stored in a cell library
 - Cell library is NOT free; you need to buy

ECE 156A

9

Structural Verilog model


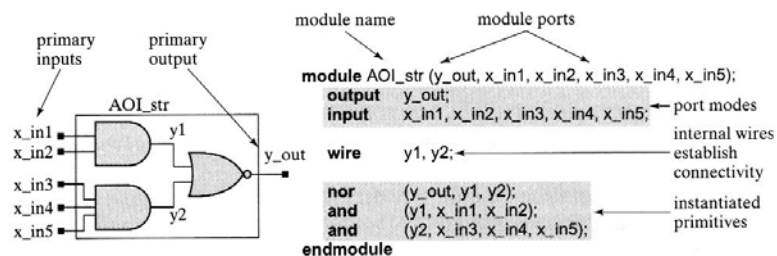


FIGURE 4-5 An AOI circuit and its Verilog structural model.

ECE 156A

10

Verilog Behavior of D FF

 

```

module Flip_flop (q, data_in,
  clk, rst);
  input data_in, clk, rst;
  output q;
  reg q;


  always @ (posedge clk)
  begin
    if (rst == 1) q = 0;
    else q = data_in;
  end
endmodule

```


Declaration of Synchronous Behavior

Procedural Statements

Block diagram view

 

Block Diagram

 

Schematic

One Implementation


Comparison

- Block vs. Implementation
 - Block view
 - Specify inputs and outputs
 - No internal detail
 - Implementation
 - Include specific detail
 - One block view can have many implementations
- Structural vs. Behavior
 - Structural model
 - Specify how a function is achieved
 - Behavior model
 - Specify only the function
 - One behavior can have many structural models

ECE 156A

13

Hierarchical design example

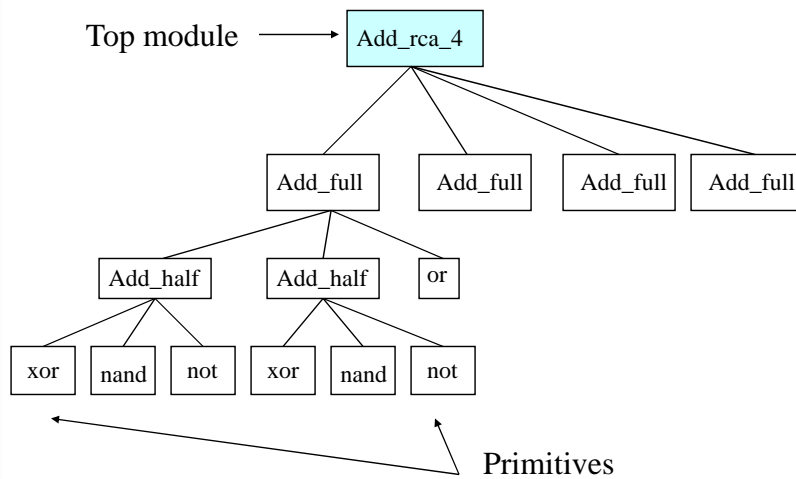

An half adder (behavior/structural)

```


module Add_half_2 (sum, c_out, a, b);
  input a, b;
  output c_out, sum;

```

```

  assign {c_out, sum} = a + b;
endmodule

```

 

```

module Add_half_1 (sum, c_out, a, b);
  input a, b;
  output sum, c_out;
  wire c_out_bar;

```

```

  xor (sum, a, b);
  nand (c_out_bar, a, b);
  not (c_out, c_out_bar);
endmodule


```



ECE 156A

15

A full adder (structural)

 

```

module Add_full (sum, c_out, a, b, c_in); // parent module
  input a, b, c_in;
  output c_out, sum;
  wire w1, w2, w3;

  Add_half M1 (w1, w2, a, b); // child module
  Add_half M2 (sum, w3, w1, c_in); // child module
  or (c_out, w2, w3); // primitive instantiation
endmodule

```

ECE 156A

16

4-bit adder

Module Add_full(sum, c_out, a, b, c_in)

```
module array_of_adders (sum, c_out, a, b, c_in);
    input  [3:0]  a,b;
    input                c_in;
    output [3:0]  sum;
    output [3:0]  c_out;
    wire   [3:1]  carry;
```

```
    Add_full M [3:0] (sum, {c_out, carry[3:1]}, a, b, {carry[3:1], c_in});
```

```
endmodule
```

Same as saying ...

```
Add_full M[0](sum[0], carry[1], a[0], b[0], c_in)
Add_full M[1](sum[1], carry[2], a[1], b[1], carry[1])
Add_full M[2](sum[2], carry[3], a[2], b[2], carry[2])
Add_full M[3](sum[3], c_out, a[3], b[3], carry[3])
```

Behavior model of a 4-bit adder

```
module adder_4_RTL (a, b, c_in, sum, c_out);
```

```
    output [3:0]  sum;
```


```
    output                c_out;
```

```
    input  [3:0]  a, b;
```


```
    input                c_in;
```

```
    assign {c_out, sum} = a + b + c_in;
```

```
endmodule
```

 

16-bit adder

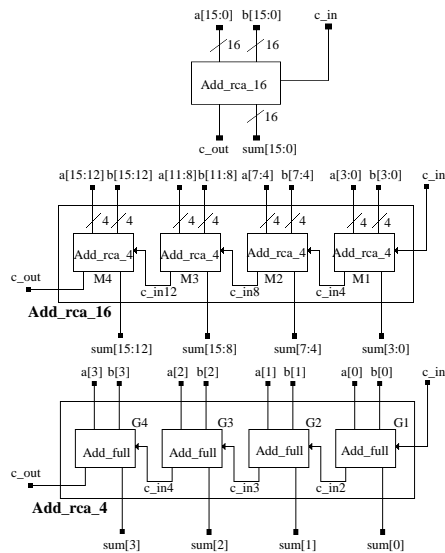

ECE 156A

19

16-bit Adder

```

module Add_rca_16 (sum, c_out, a, b, c_in);
  output [15:0] sum;
  output c_out;
  input [15:0] a, b;
  input c_in;
  wire c_in, c_in4, c_in8, c_in12, c_out;

  Add_rca_4 M1 (sum[3:0], c_in4, a[3:0], b[3:0], c_in);
  Add_rca_4 M2 (sum[7:4], c_in8, a[7:4], b[7:4], c_in4);
  Add_rca_4 M3 (sum[11:8], c_in12, a[11:8], b[11:8], c_in8);
  Add_rca_4 M4 (sum[15:12], c_out, a[15:12], b[15:12], c_in12);
endmodule

module Add_rca_4 (sum, c_out, a, b, c_in);
  output [3:0] sum;
  output c_out;
  input [3:0] a, b;
  input c_in;
  wire c_in4, c_in3, c_in2;

  Add_full G1 (sum[0], c_in2, a[0], b[0], c_in);
  Add_full G2 (sum[1], c_in3, a[1], b[1], c_in2);
  Add_full G3 (sum[2], c_in4, a[2], b[2], c_in3);
  Add_full G4 (sum[3], c_out, a[3], b[3], c_in4);
endmodule
  
```

The concept of *Design Entry*

- Design Entry
 - The entry point to do your design
 - Select design data representation(s)
 - Behavior, RTL, Gate-Transistor Schematics
- Schematic
 - Draw your design with gates/transistors/lines
 - For high-performance blocks
- Hardware Description Language
 - Describe your design with Verilog/VHDL
 - Just like writing a program
 - No need to worry about structural detail

ECE 156A

21

Unit level verification

- Each block or unit should be verified through extensive testbench simulation

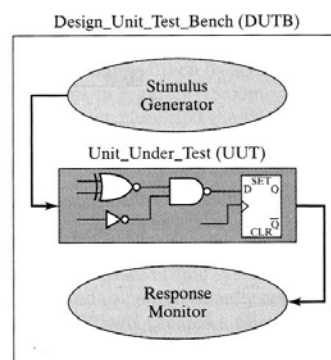


FIGURE 4-16 Organization of a testbench for verifying a unit under test.

ECE 156A

22

A testbench example

```

module t_Add_half();
  wire      sum, c_out;
  reg       a, b;
  Add_half_0_delay M1 (sum, c_out, a, b); //UUT
  initial begin // Time Out
    #100 $finish;
  end
  end
  initial begin // Stimulus patterns
    #10 a = 0; b = 0;
    #10 b = 1;
    #10 a = 1;
    #10 b = 0;
  end
endmodule

```

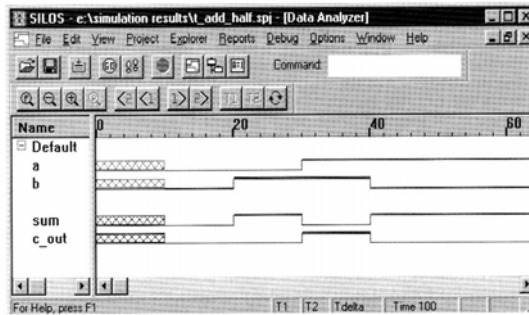


FIGURE 4-17 Waveforms produced by a simulation of *Add_half_0_Delay*, a 0-delay binary half adder.

ECE 156A

23

Generic testbench design

```

module t_DUTB_name (); // substitute the name of the UUT
  reg ...; // Declaration of register variables for primary
           // inputs of the UUT
  wire ...; // Declaration of primary outputs of the UUT
  parameter time_out = // Provide a value

  UUT_name M1_instance_name (UUT ports go here);
  initial $monitor ( // Specification of signals to be monitored and
                    // displayed as text
    #time_out $stop; // Stopwatch to assure termination of simulation
  initial // Develop one or more behaviors for pattern
           // generation and/or
           // error detection

  begin // Behavioral statements generating waveforms
        // to the input ports, and comments documenting
        // the test. Use the full repertoire of behavioral
        // constructs for loops and conditionals.

  end
endmodule

```

- New version of Verilog has a lot more features to support testbench development

ECE 156A

24

Delay model in verilog

```
module Add_half_1 (sum, c_out, a, b);  
  input  a, b;  
  output sum, c_out;  
  wire  c_out_bar;  
  
  xor #2 (sum, a, b);  
  nand #2 (c_out_bar, a, b);  
  not #1 (c_out, c_out_bar);  
endmodule
```

- These delays *have no physical meaning*
 - They are used only for simulation
 - The ordering of events is what being specified
 - Not the actual timing
 - Relative delays are more important than absolute numbers

ECE 156A

25

Cell Delay Characterization

```
module and123 (o, a, b);  
  input  a, b;  
  output o;  
  and (o, a, b);  
  
  specify  
    specparam  
      Tpd_0_1 = 1.13, 3.09, 7.75  
      Tpd_1_0 = 0.93, 2.50, 7.34  
      (a => o) = (Tpd_0_1, Tpd_1_0);  
      (b => o) = (Tpd_0_1, Tpd_1_0);  
  endspecify  
endmodule
```

- The delays are only estimations
 - Maybe from SPICE simulation of the actual layout
- This can only be done for very small cells

ECE 156A

26

Inertial delay concept

 


FIGURE 4-20 Event de-scheduling caused by an inertial delay.

- In the upper example, the event of rising transition is de-scheduled by the simulator because the pulse width is less than the propagation delay

ECE 156A

27

User-defined primitives

- Basic constructs in your design
- Contain detailed table-like description
- Use the keywords
 - **primitive**
 - **endprimitive**
- Differentiate themselves from Modules
 - In test, verification, and simulation, never goes inside primitives (black-boxes)

User-defined primitives

- Instantiated in the same manner as **and**, **or**, **not**, **nor**, **nand**, etc.
- Always has one output port!*
- Output port must be declared as **net** in a combinational primitive
- Output port must be declared as **reg** in a sequential primitive
- No **inout**
- Specify everything (anything left unspecified will be treated as X)

2-bit multiplexer


- Z input is treated as X!

```

primitive mux_prim (mux_out, select, a, b);
  output mux_out;
  input  select, a, b;
  table
// select  a      b      : mux_out
  0  0  0      : 0; // Table order = port order
  0  0  1      : 0; // One output, multiple inputs, no inout
  0  0  x      : 0; // Only 0, 1, x on input and output
  0  1  0      : 1; // A z input in simulation is treated as x
  0  1  1      : 1; // Last column is the output
  0  1  x      : 1;

// select  a      b      : mux_out
  1  0  0      : 0;
  1  1  0      : 0;
  1  x  0      : 0;
  1  0  1      : 1;
  1  1  1      : 1;
  x  x  1      : 1;
  x  0  0      : 0; // Reduces pessimism
  x  1  1      : 1;
  endtable
endprimitive
  
```

 // Note: Combinations not explicitly specified will drive "x" under simulation



Shorthand notation “?”

table

// Shorthand notation;
// ? represents iteration of the table entry over the values 0, 1, x.
// i.e., don't care on the input

```
// select      a      b      : mux_out
      0      0      ?      : 0; // ? = 0, 1, x shorthand notation
      0      1      ?      : 1;

      1      ?      0      : 0;
      1      ?      1      : 1;

      ?      0      0      : 0;
      ?      1      1      : 1;
endtable
```

Primitive notations


- 0, 1, x:
- ? : {0, 1, x}
- b : {0, 1}
- - : no change
- (vw) : $v \in \{0, 1, x\} \rightarrow w \in \{0, 1, x\}$
- * : {0, 1, x} \rightarrow {0, 1, x}
- r : (01)
- f : (10)
- p : (01), (0x), (x1), (0z), (z1)
- n : (10), (1x), (x0), (1z), (z0)

Sequential Primitives

- n inputs
- 1 state and 1 output
- n+2 columns
 - <n inputs>, <state>, <output>=<next state>
- Two types:
 - Level sensitive
 - Achieve transparent latch (a latch can be made “invisible”)
 - Edge sensitive

A Transparent Latch
 
```
primitive latch (q_out, enable, data);
output q_out;
input enable, data;
reg q_out;
```




```
table
// en  data      state: q_out/next state
  1    1      :    ? :    1;
  1    0      :    ? :    0;
  0    ?      :    ? :    -;
```

// Note: '-' denotes "no change."

// The state is the residual value of q_out

```
endtable
endprimitive
```

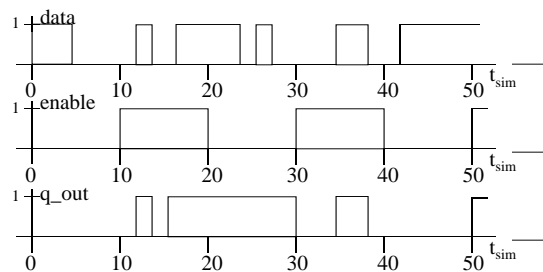// Note: Combinations not explicitly specified will drive "x"
// under simulation




Rising Edge-Sensitive Latch

```
primitive d_prim1 (q_out, clock, data);
output q_out;
input clock, data;
```

```
reg q_out;
```

```
table
// clock data state : q_out/next state
(01) 0 : ? : 0; // Rising clock edge
(01) 1 : ? : 1;
(0x) ? : ? : X;
(?0) ? : ? : -; // Falling clock edge

 
? (??) : ? : -; // Steady clock,
ignore data
endtable
endprimitive
```



Level-S Dominates Edge-S

```
primitive jk_prim (q_out, clock, j, k, preset, clear);
output q_out;
input clock, j, k, preset, clear;
reg q_out;

table
// clk j k pre cir state q_out/next_state
// Preset Logic
? ? ? 0 1 : ? : 1;
? ? ? * 1 : 1 : 1;
// Clear Logic
? ? ? 1 0 : ? : 0;
? ? ? 1 * : 0 : 0;
// Normal Clocking
// clk j k pre cir state q_out/next_state
r 0 0 0 0 : 0 : 1;
r 0 0 1 1 : ? : -;
r 0 1 1 1 : ? : 0;
r 1 0 1 1 : ? : 1;
r 1 1 1 1 : 0 : 1;
r 1 1 1 1 : 1 : 0;
f ? ? ? ? : ? : -;
// j and k cases
// clk j k pre cir state q_out/next_state
b * ? ? ? : ? : -;
b ? * ? ? : ? : -;
p 0 0 1 1 : ? : -;
p 0 ? 1 ? : 0 : -;
p ? 0 ? 1 : 1 : -;
(?0) ? ? ? ? : ? : -;
(1x) 0 0 1 1 : ? : -;
(1x) 0 ? 1 ? : 0 : -;
(1x) ? 0 ? 1 : 1 : -;
x * 0 ? 1 : 1 : -;
x 0 * 1 ? : 0 : -;
endtable
endprimitive
```

 

Summary

- Each row specify a transition on only 1 input
- All no-effect transitions should be stated or the results will be X
- Only 0,1,x,- are allowed for outputs (no ?)
- Z is X in a primitive
- Input order = specification order

State initialization

- You can use the “initial” command
- In reality, it won't initialize itself
- You better not count on it in real implementation

```
primitive d_prim2 (q_out, clock, data);
  output q_out;
  input  clock, data;

  reg    q_out;
  initial q_out = 0; // Optional -- Declares
                    // initial value of q_out

  table
  //  clk    data    state : q_out/next state
  (01)  0      : ?    : 0;           // Rising clock edge
  (01)  1      : ?    : 1;
  (0?)  1      : 1    : 1;

  (?0)  ?      : ?    : -;           // Falling clock edge

  ?     (??)   : ?    : -;           // Steady clock, ignore data
  endtable
endprimitive
```